

# Sequential Logic Design

- Latches and Flip-Flops
- Synchronous Logic Design
- Finite State Machines
- Timing of Sequential Logic
- Parallelism





Chap 3

# Sequential Circuits



- Outputs of sequential logic depend on current and prior input values – it has memory
  - Use **feedback from output to input** to store information
- Some definitions:
  - **State** : all the information about a circuit necessary to explain its future behavior
  - **Latches and flip-flops** : state elements that store one bit of state
    - » Bistable circuit
    - » SR Latch
    - » D Latch
    - » D Flip-flop
  - **Synchronous sequential circuits** : combinational logic followed by a bank of flip-flops
  
# Bistable Circuit

- Fundamental building block of other state elements
- Two outputs:  $Q, \bar{Q}$
- No inputs to control the state




  - Consider the two possible cases :
  - $Q = 0$ :
    - » then  $Q = 0, \bar{Q} = 1$  (consistent)
  - $Q = 1$ :
    - » then  $Q = 1, \bar{Q} = 0$  (consistent)




# SR (Set/Reset) Latch

- SR Latch

 



- Consider the four possible cases :

 - $S = 1, R = 0$ 
  - » Set the output
- $S = 0, R = 1$ 
  - » Reset the output
- $S = 0, R = 0$ 
  - »  $Q = Q_{prev}$  : Memory
- $S = 1, R = 1$ 
  - »  $Q = 0, \bar{Q} = 0$  : Invalid state



$Q_{prev} = 0$



$Q_{prev} = 1$

  

# D Latch





- Two inputs : CLK, D
  - **CLK**: controls when the output changes
  - **D** (the data input): controls what the output changes to
- Function
  - When CLK = 1,
    - » D passes through to Q (transparent)
  - When CLK = 0,
    - Q holds its previous value (opaque)
- Avoids invalid case

D Latch  
Symbol

  

$CLK$	$D$	$\overline{D}$	$S$	$R$	$Q$	$\overline{Q}$
0	X	$\overline{X}$	0	0	$Q_{prev}$	$\overline{Q}_{prev}$
1	0	1	0	1	0	1
1	1	0	1	0	1	0


- D Latch CMOS Implementation

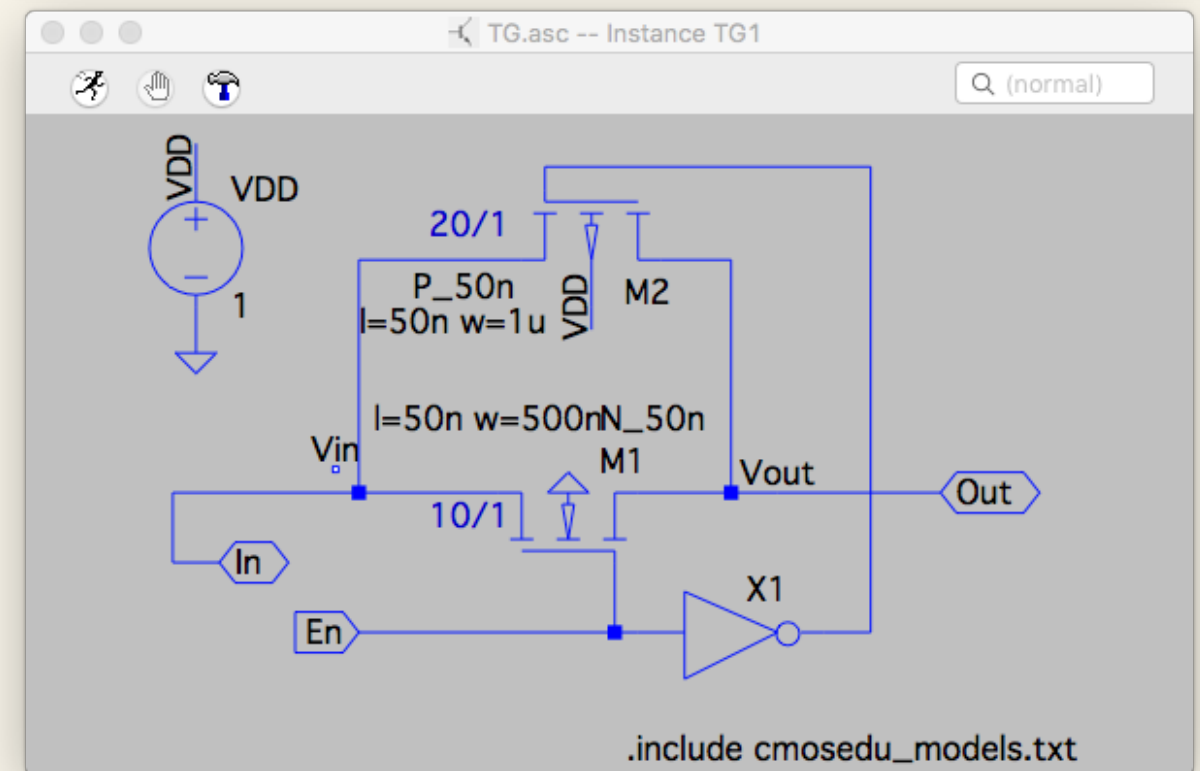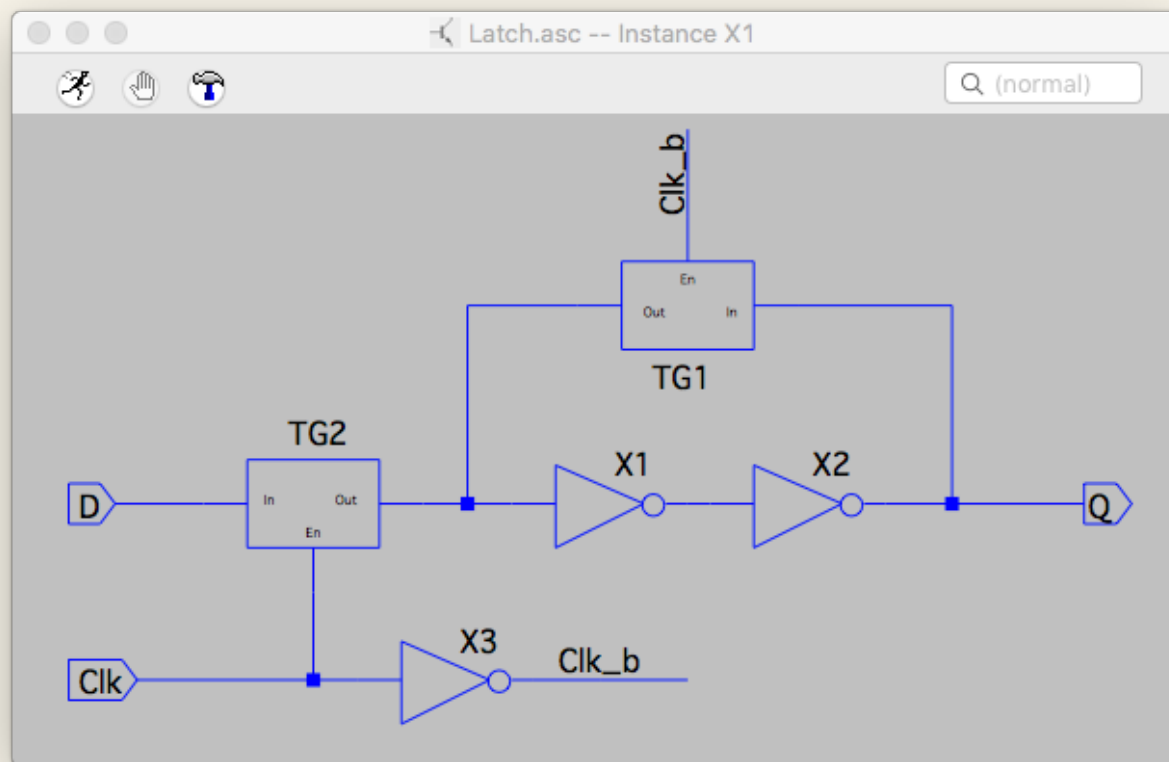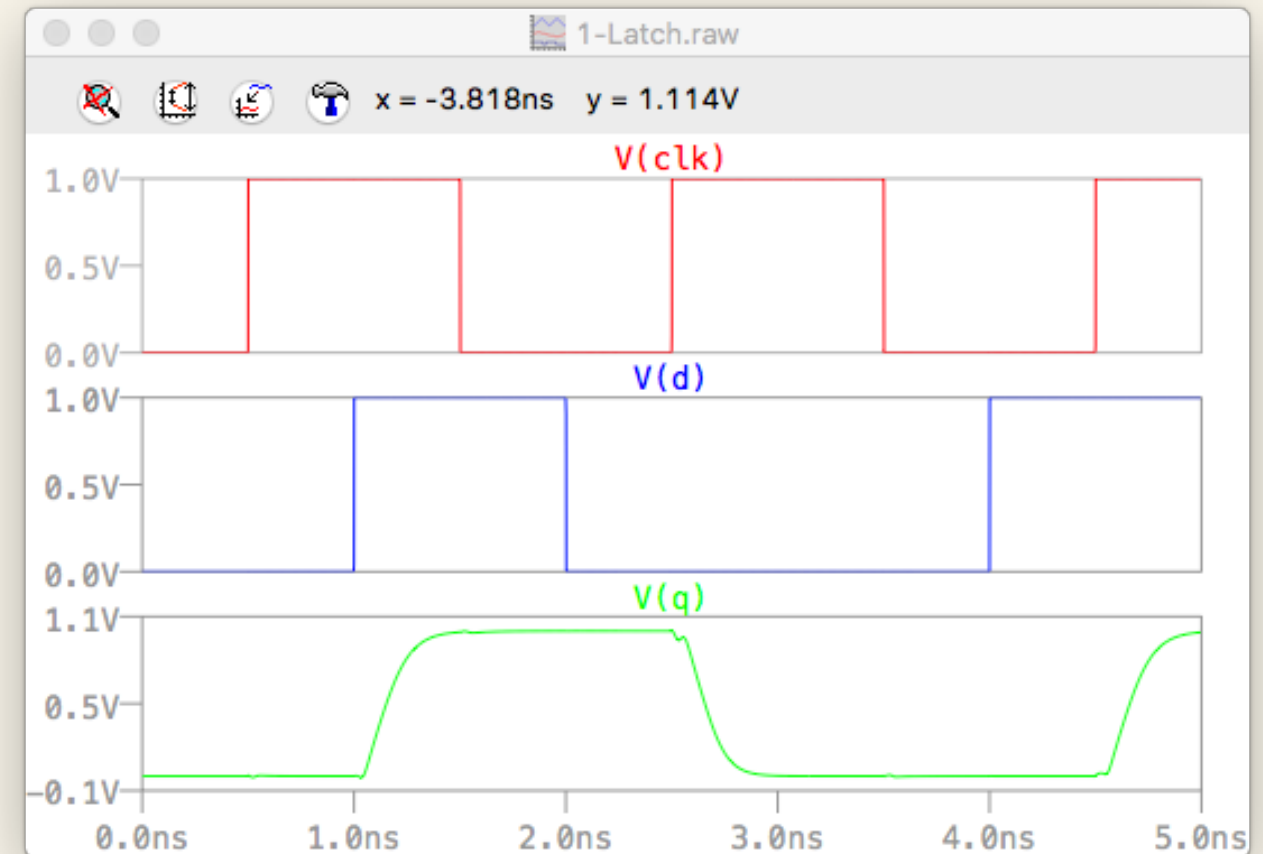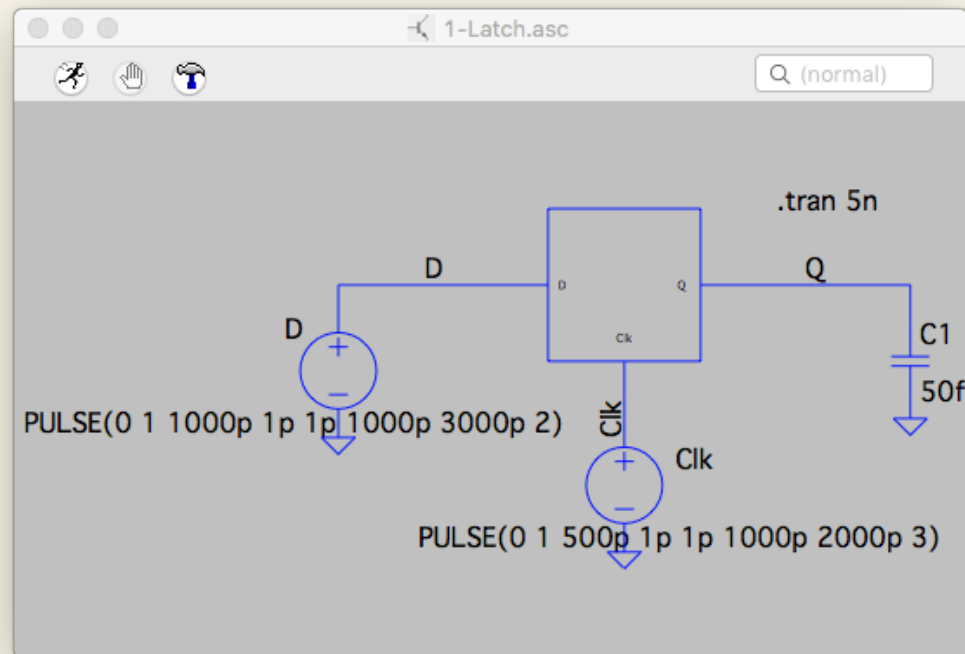

# D Flip-Flop

- Inputs: CLK, D
- Function
  - Samples D on **rising edge of CLK**
    - » When CLK rises from 0 to 1, D passes through to Q
    - » Otherwise, Q holds its previous value
  - Q changes only on rising edge of CLK
- Called **edge-triggered**
- Activated on the clock edge

D Flip-Flop  
Symbols

 

- D Flip-Flop Internal Circuit


- Two back-to-back latches (L1 and L2) controlled by complementary clocks

- » When CLK = 0

- L1 is transparent
      - L2 is opaque
      - D passes through to N1

- » When CLK = 1



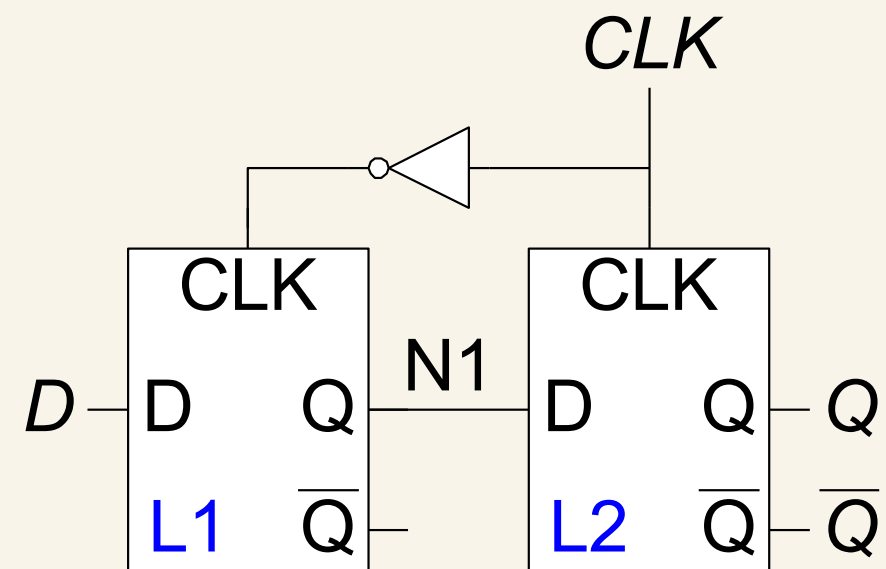
- L2 is transparent
      - L1 is opaque
      - N1 passes through to Q





- Thus, on the edge of the clock (when CLK rises from 0 to 1)
      - D passes through to Q




- D Flip-Flop CMOS Implementation

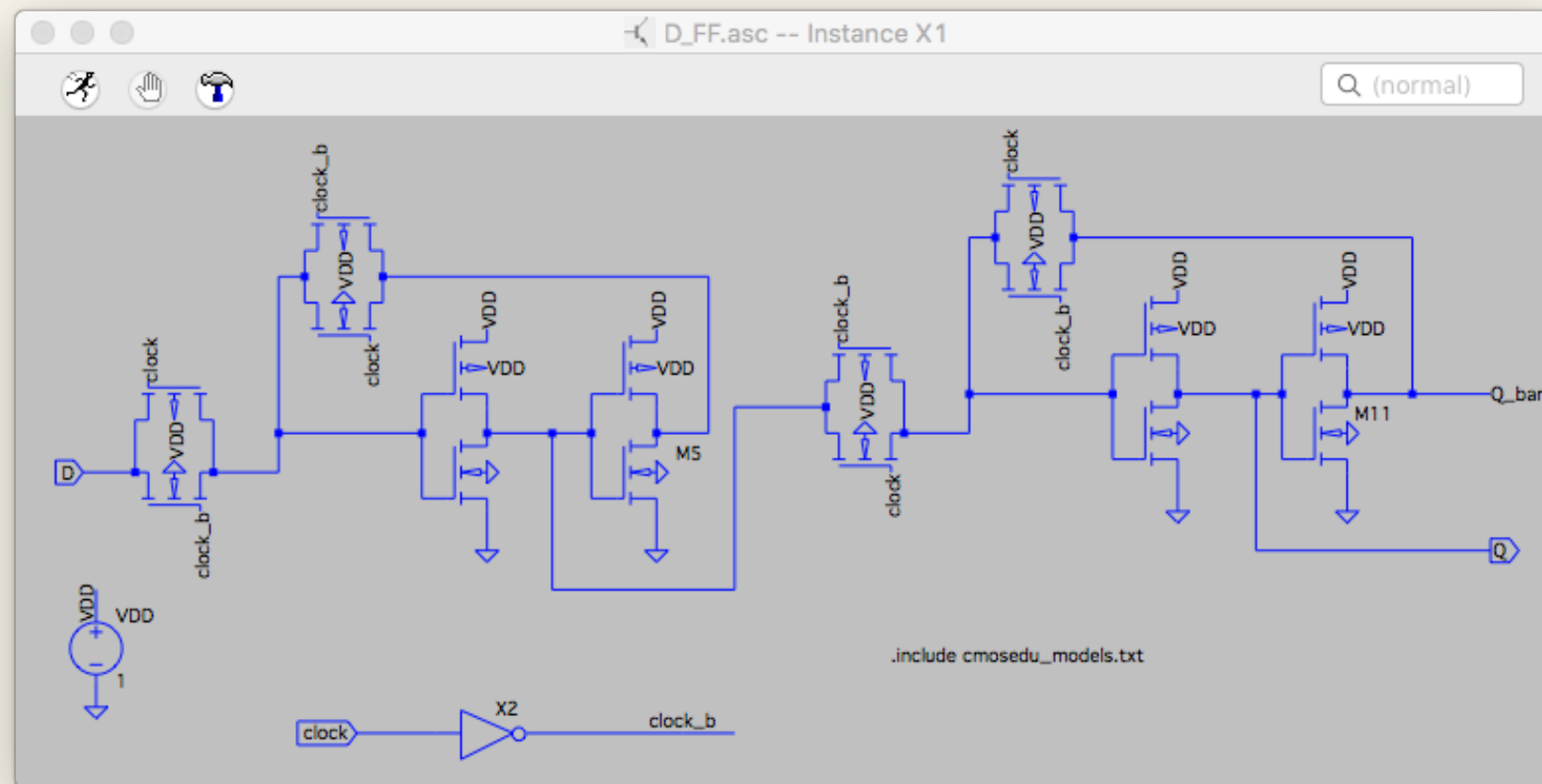 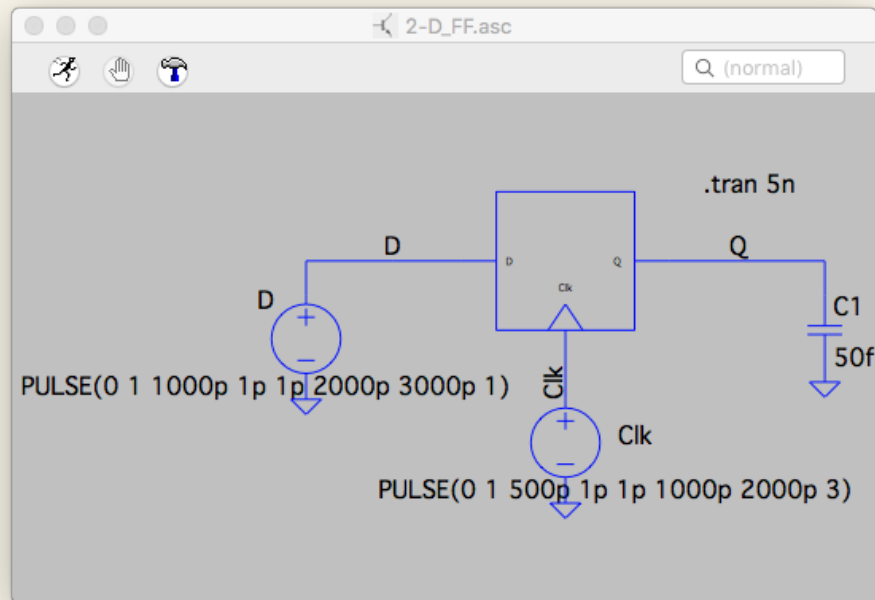

# D Latch vs. D Flip-Flop

  


# Registers: Multi-bit Flip-Flop

 
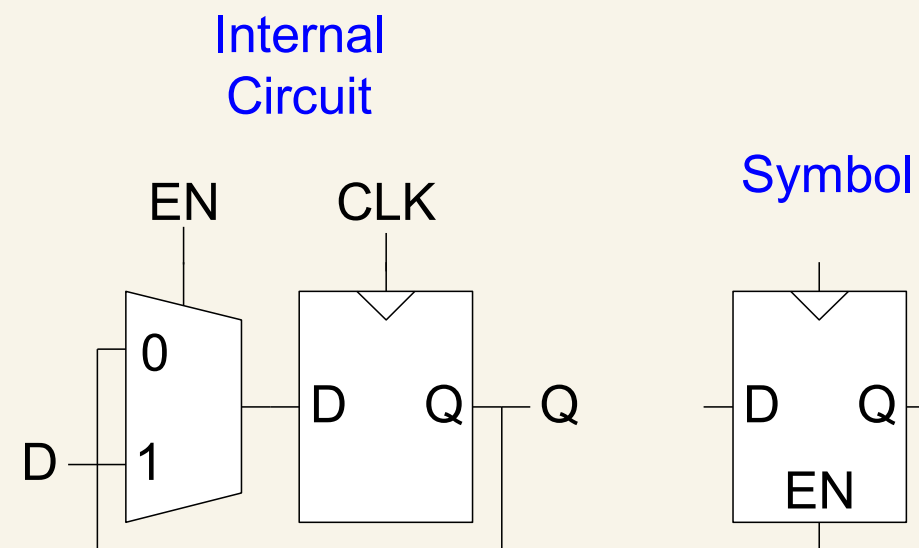
# Enabled Flip-Flops


- Inputs: **CLK, D, EN**
  - The enable input (EN) controls when new data (D) is stored
- Function
  - $EN = 1$  : D passes through to Q on the clock edge
  - $EN = 0$  : the flip-flop retains its previous state




# Resettable Flip-Flops

- Inputs : **CLK, D, Reset**
  - Reset = 1 : Q is forced to 0
  - Reset = 0 : flip-flop behaves as ordinary D flip-flop
- Two types :
  - **Asynchronous** : resets immediately when Reset = 1
    - » requires changing the internal circuitry of the flip-flop
  - **Synchronous** : resets at the clock edge only

Symbols

 


Internal  
Circuit

 

# Settable Flip-Flops


- Inputs : CLK, D, Set
- Function :
  - Set = 1: Q is set to 1
  - Set = 0: the flip-flop behaves as ordinary D flip-flop

## Symbols

 

 
# Sequential Logic

- Sequential circuits: all circuits that aren't combinational
- A problematic circuit:



 - » No inputs and 1-3 outputs
- » Astable circuit, oscillates
- » Period depends on inverter delay
- » It has a cyclic path: output fed back to input




# Synchronous Sequential Logic Design

- Breaks cyclic paths by inserting **registers**
- Registers contain **state** of the system
- State changes at clock edge : system **synchronized** to the clock
- Rules of synchronous sequential circuit composition
  - » Every circuit element is either a register or a combinational circuit
  - » At least one circuit element is a register
  - » All registers receive the same clock signal
  - » Every cyclic path contains at least one register
- Two common synchronous sequential circuits
  - » Finite State Machines (FSMs)
  - » Pipelines



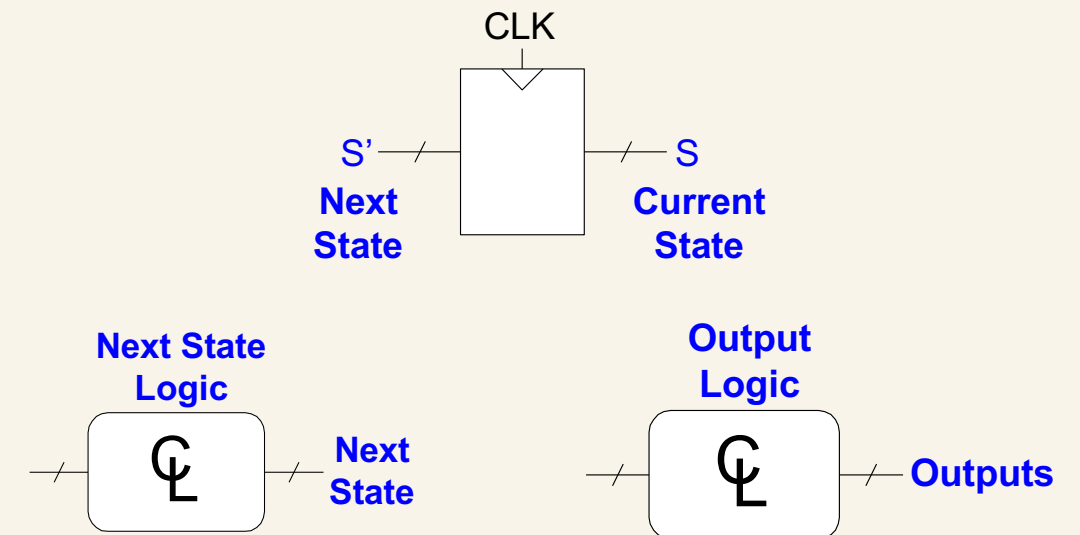
# Finite State Machine (FSM)


- Consists of:
  - State register
    - » Stores current state
    - » Loads next state at clock edge
  - Combinational logic
    - » Computes the next state
    - » Computes the outputs
- Next state determined by current state and inputs
- Two types of finite state machines differ in output logic:
  - » **Moore FSM**: outputs depend only on current state
  - » **Mealy FSM**: outputs depend on current state and inputs



Moore FSM

 



Mealy FSM

 


 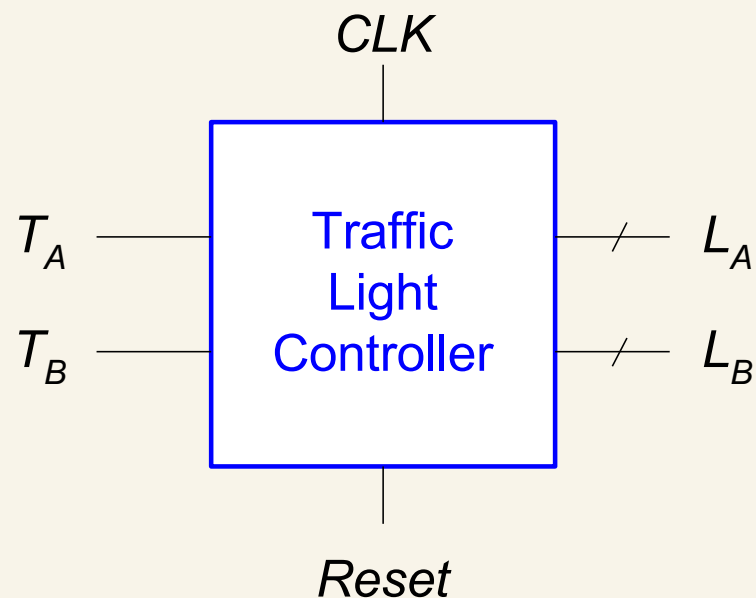
# FSM Example

- Traffic light controller
  - » Traffic sensors:  $T_A$ ,  $T_B$  (TRUE when there's traffic)
  - » Lights:  $L_A$ ,  $L_B$
- FSM Black Blox




- FSM State Transition Diagram

- » Moore FSM: outputs labeled in each state
- » States : Circles
- » Transitions : Arcs

- FSM State Transition Diagram

Current State	Inputs		Next State
$S$	$T_A$	$T_B$	$S'$
S0	0	X	S1
S0	1	X	S0
S1	X	X	S2
S2	X	0	S3
S2	X	1	S2
S3	X	X	S0

 

- FSM Encoded State Transition Table

Current State		Inputs		Next State	
$S_1$	$S_0$	$T_A$	$T_B$	$S'_1$	$S'_0$
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

$$S'_1 = S_1 \oplus S_0$$

$$S'_0 = \overline{S_1}\overline{S_0}\overline{T_A} + S_1\overline{S_0}\overline{T_B}$$

- FSM Output Table

Current State		Outputs			
$S_1$	$S_0$	$L_{A1}$	$L_{A0}$	$L_{B1}$	$L_{B0}$
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

Output	Encoding
green	00
yellow	01
red	10

$$L_{A1} = S_1$$


$$L_{A0} = \overline{S_1}S_0$$

$$L_{B1} = \overline{S_1}$$


$$L_{B0} = S_1S_0$$

- FSM Schematic


- State Register

 



- Next State Logic

 

- Output Logic

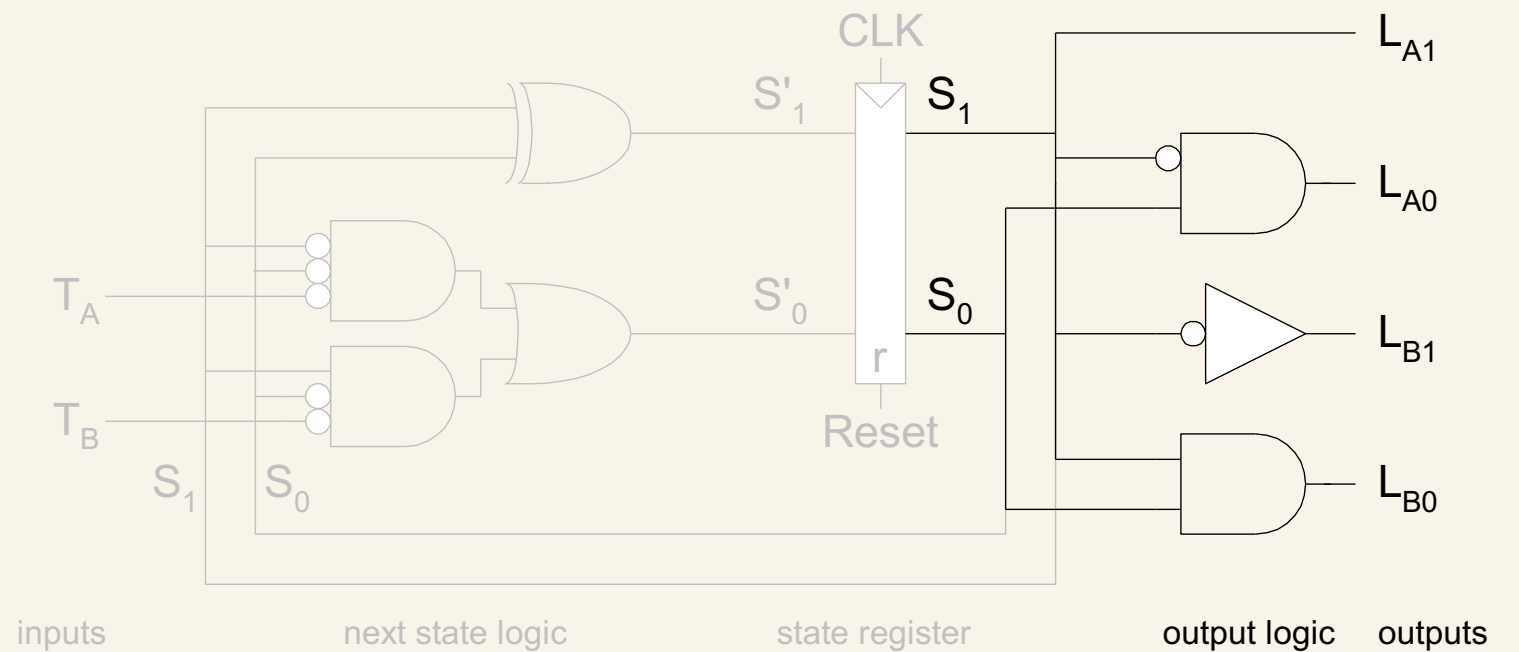

- FSM Timing Diagram

  

# FSM State Encoding

- **Binary** encoding:
  - i.e., for four states, 00, 01, 10, 11
- **One-hot** encoding
  - One state bit per state
  - Only one state bit HIGH at once
    - » i.e., for 4 states, 0001, 0010, 0100, 1000
  - Requires **more flip-flops**
  - Often next state and output **logic is simpler**




# Moore vs. Mealy FSM


- Example
  - » You have a snail that crawls down a paper tape with 1's and 0's on it. The snail smiles whenever the last two digits it has crawled over are 01. Design Moore and Mealy FSMs of the snail's brain.
- State Transition Diagrams



## Moore FSM

 

## Mealy FSM

 

- Moore Tables

» Transition Table

Current State		Inputs	Next State	
$S_1$	$S_0$	$A$	$S'_1$	$S'_0$
0	0	0	0	1
0	0	1	0	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0

State	Encoding
S0	00
S1	01
S2	10

$$S'_1 = S_0 A$$

$$S'_0 = \overline{A}$$

» Output Table

Current State		Output
$S_1$	$S_0$	$Y$
0	0	0
0	1	0
1	0	1

$$Y = S_1$$

- Mealy Tables

» Transition Table

» Output Table


Current State	Input	Next State	Output
$S_0$	$A$	$S'_0$	$Y$
0	0	1	0
0	1	0	0
1	0	1	0
1	1	0	1

State	Encoding
S0	00
S1	01


$$S'_0 = \overline{A}$$

$$Y = S_0 A$$


- Moore Schematic

 


- Mealy Schematic

 


- Moore & Mealy Timing Diagram

 

**Moore FSM**


 



**Mealy FSM**

 
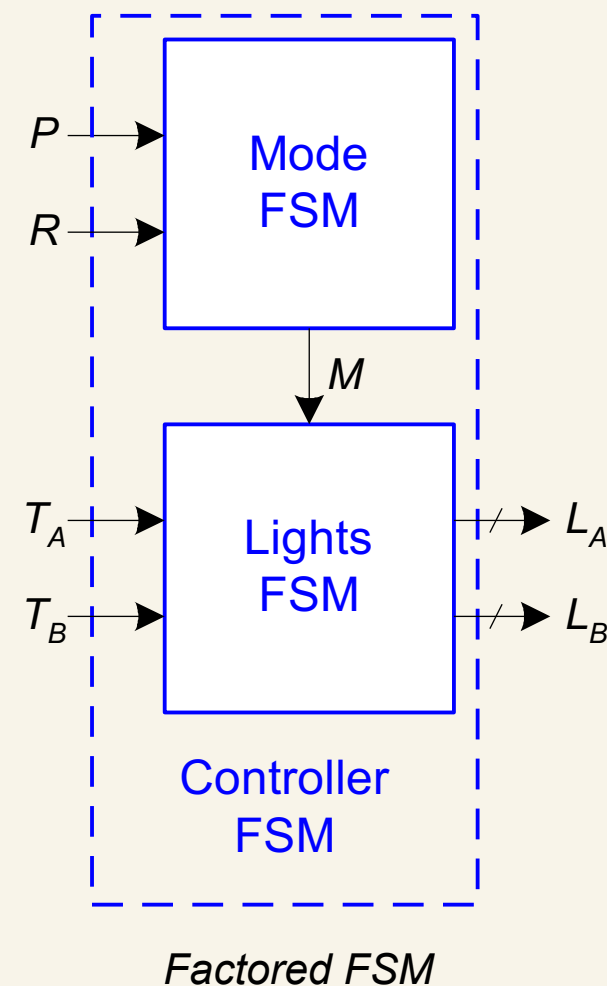 
# Factoring FSM


- Break complex FSMs into smaller interacting FSMs
- Example: Modify traffic light controller to have Parade Mode.
  - Two more inputs: P, R
  - When P = 1, enter Parade Mode & Bravado Blvd light stays green
  - When R = 1, leave Parade Mode



 


Lights FSM

Factored FSM

 

Mode FSM

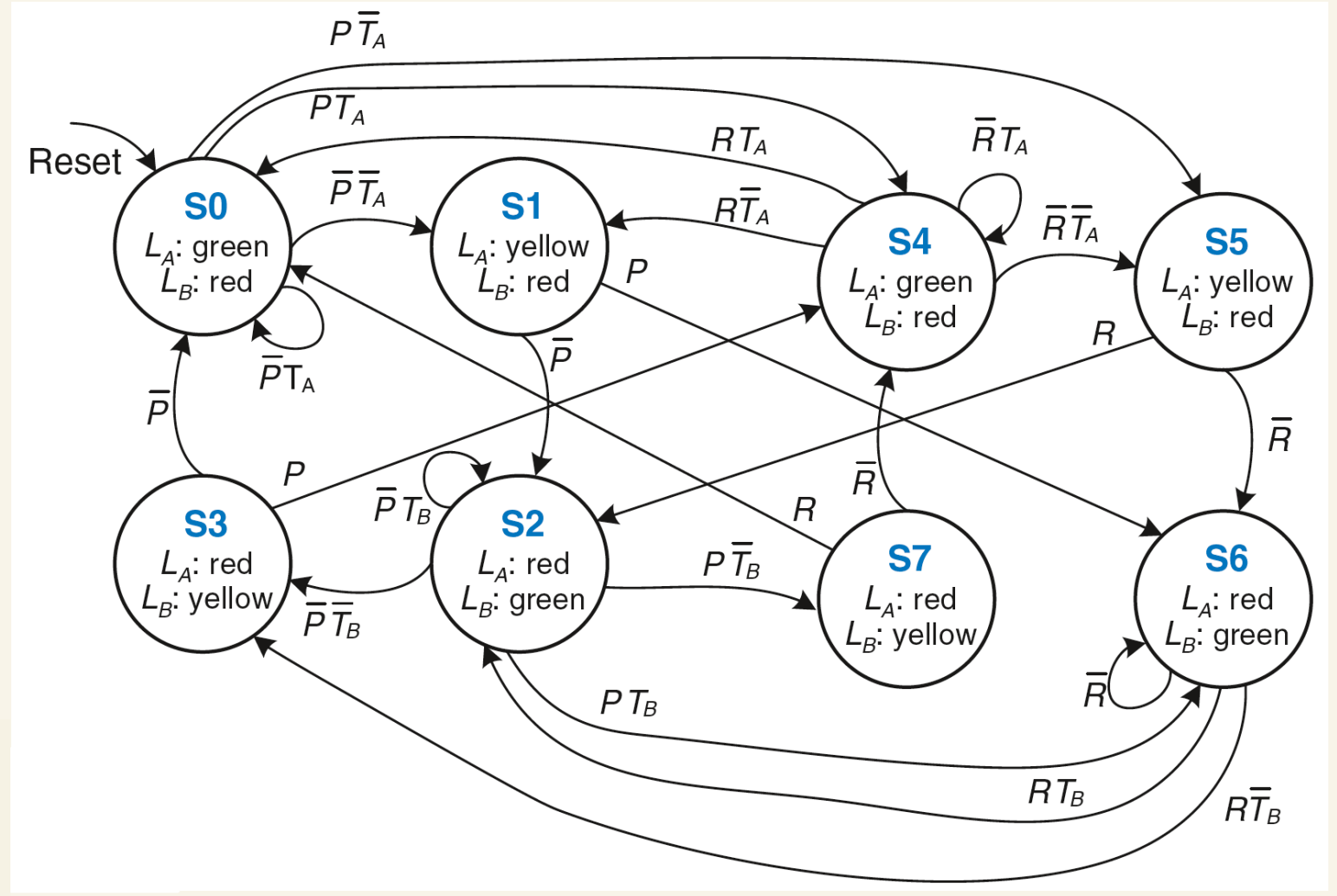

Unfactored FSM

# FSM Design Procedure

1. Identify inputs and outputs
2. Sketch state transition diagram
3. Write state transition table
4. Select state encodings
5. For Moore machine:
  - Rewrite state transition table with state encodings
  - Write output table
6. For a Mealy machine:
  - Rewrite combined state transition and output table with state encodings
7. Write Boolean equations for next state and output logic
8. Simplify Boolean equations
9. Sketch the circuit schematic

# Timing


- Flip-flop samples D at clock edge
- D must be stable when sampled
- Similar to a photograph, D must be stable around clock edge
- If not, metastability can occur


 
# Timing Constraints


- Input Constraints

- » **Setup time:**  $t_{\text{setup}}$  = time before clock edge data must be stable (i.e. not changing)
- » **Hold time:**  $t_{\text{hold}}$  = time after clock edge data must be stable
- » **Aperture time:**  $t_a$  = time around clock edge data must be stable ( $t_a = t_{\text{setup}} + t_{\text{hold}}$ )




- Output Constraints

 - » **Propagation delay:**  $t_{\text{pcq}}$  = time after clock edge that the output Q is guaranteed to be stable (i.e., to stop changing)
- » **Contamination delay:**  $t_{\text{ccq}}$  = time after clock edge that Q might be unstable (i.e., start changing)


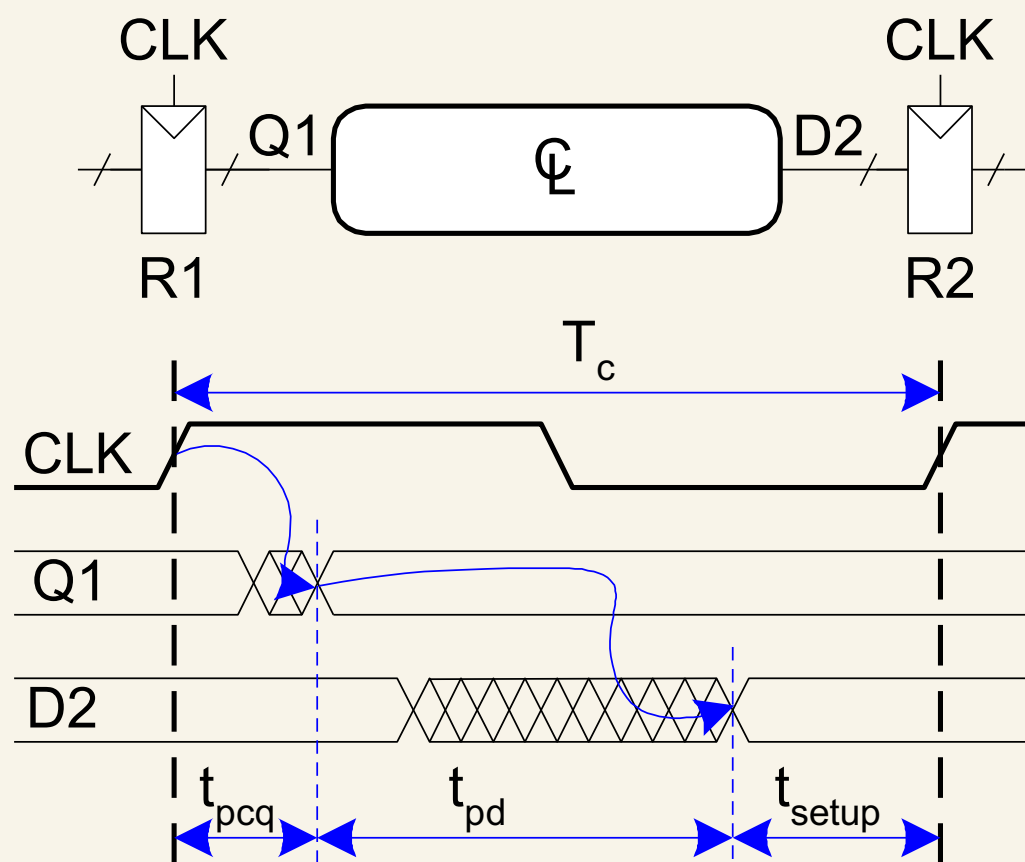
# Setup Time Constraint

- Depends on the **maximum** delay from register R1 through combinational logic to R2
- The input to register R2 must be stable at least  $t_{\text{setup}}$  before clock edge




$$T_c \geq t_{pcq} + t_{pd} + t_{\text{setup}}$$
$$t_{pd} \leq T_c - (t_{pcq} + t_{\text{setup}})$$

$(t_{pcq} + t_{\text{setup}})$ : sequencing overhead
 
# Hold Time Constraint


- Depends on the **minimum** delay from register R1 through the combinational logic to R2
- The input to register R2 must be stable for at least  $t_{\text{hold}}$  after the clock edge



$$t_{\text{hold}} < t_{ccq} + t_{cd}$$

$$t_{cd} > t_{\text{hold}} - t_{ccq}$$

# Timing Analysis

 

## Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

$$\text{per gate} \left[ \begin{array}{ll} t_{pd} & = 35 \text{ ps} \\ t_{cd} & = 25 \text{ ps} \end{array} \right]$$

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$t_{cd} = 25 \text{ ps}$

### Setup time constraint:

$$T_c \geq (50 + 105 + 60) \text{ ps} = 215 \text{ ps}$$


$$f_c = 1/T_c = 4.65 \text{ GHz}$$

**Hold time constraint:**

$$t_{ccq} + t_{cd} > t_{hold} ?$$

$(30 + 25) \text{ ps} > 70 \text{ ps}$  ? **No!**

## Add buffers to the short paths:

 

## Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

$$\text{per gate} \left[ \begin{array}{ll} t_{pd} & = 35 \text{ ps} \\ t_{cd} & = 25 \text{ ps} \end{array} \right]$$

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} = 2 \times 25 \text{ ps} = 50 \text{ ps}$$

### Setup time constraint:

$$T_c \geq (50 + 105 + 60) \text{ ps} = 215 \text{ ps}$$

$$f_c = 1/T_c = 4.65 \text{ GHz}$$

**Hold time constraint:**

$$t_{ccq} + t_{cd} > t_{hold} ?$$


$(30 + 50) \text{ ps} > 70 \text{ ps}$  ? **Yes!**

# Parallelism

- Two types of parallelism:
  - Spatial parallelism
    - » duplicate hardware performs multiple tasks at once
  - Temporal parallelism
    - » task is broken into multiple stages
    - » also called pipelining
    - » for example, an assembly line
- Some definitions
  - Token : Group of inputs processed to produce group of outputs
  - Latency : Time for one token to pass from start to end
  - Throughput : Number of tokens produced per unit time
- Parallelism increases throughput


- Example
  - Ben Bitdiddle bakes cookies to celebrate traffic light controller installation
  - 5 minutes to roll cookies
  - 15 minutes to bake
  - What is the latency and throughput without parallelism?
    - » Latency = 5 + 15 = 20 minutes =  $1/3$  hour
    - » Throughput = 1 tray /  $1/3$  hour = 3 trays/hour
  - What is the latency and throughput if Ben uses parallelism?
    - » Spatial parallelism
      - Ben asks Allysa P. Hacker to help, using her own oven
    - » Temporal parallelism:
      - two stages: rolling and baking
      - He uses two trays
      - While first batch is baking, he rolls the second batch, etc.

## - Spatial Parallelism

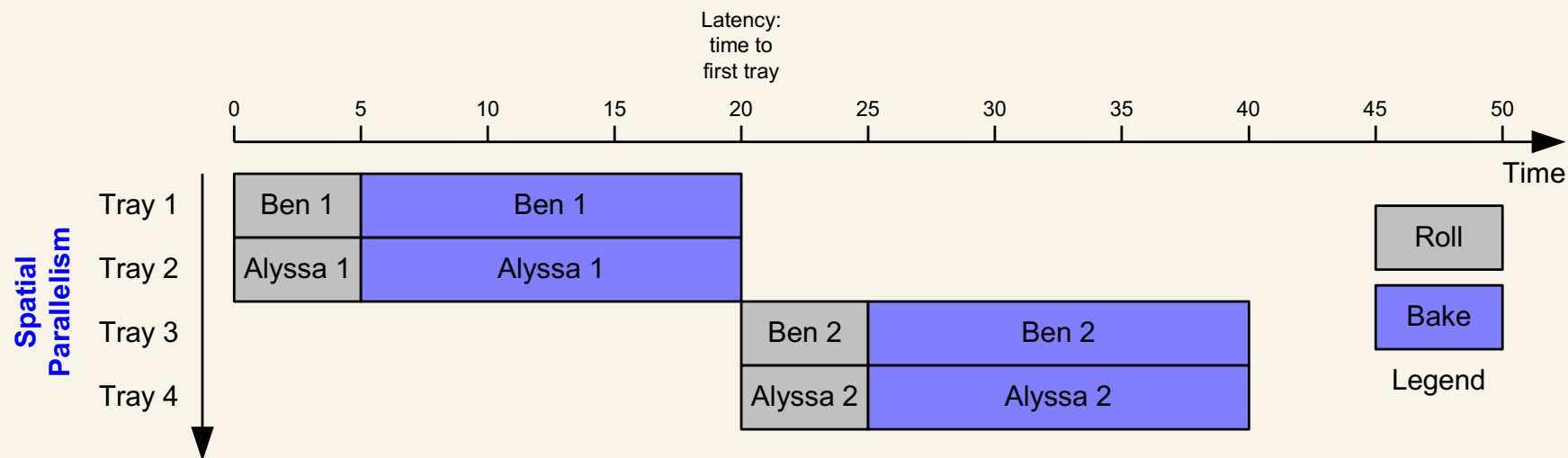

$Latency = 5 + 15 = 20 \text{ minutes} = 1/3 \text{ hour}$   
 $Throughput = 2 \text{ trays} / 1/3 \text{ hour} = 6 \text{ trays/hour}$

## - Temporal Parallelism

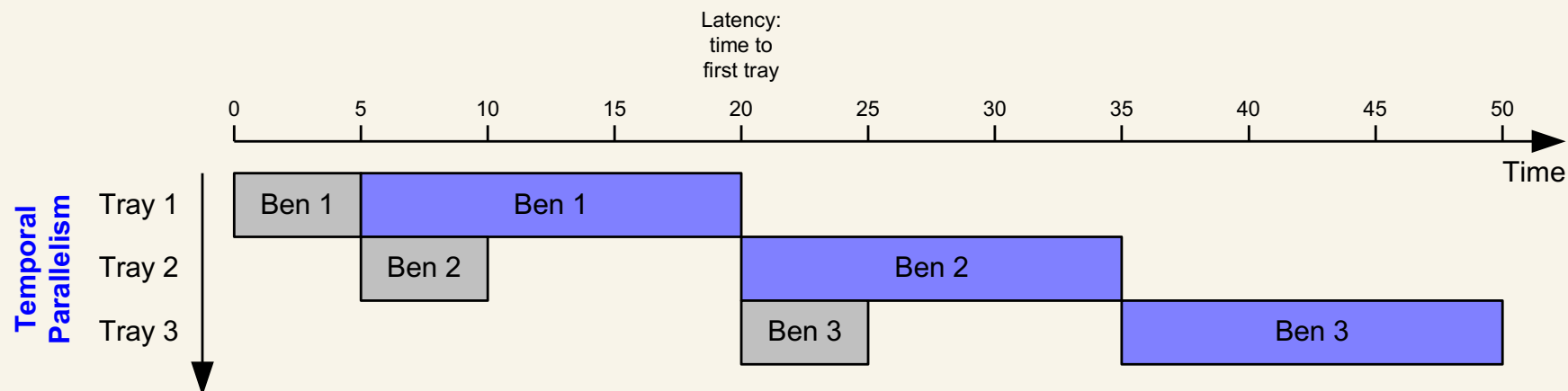

$Latency = 5 + 15 = 20 \text{ minutes} = 1/3 \text{ hour}$   
 $Throughput = 1 \text{ trays} / 1/4 \text{ hour} = 4 \text{ trays/hour}$