 





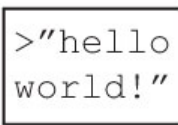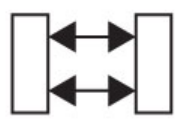
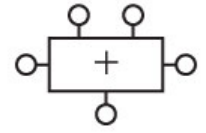
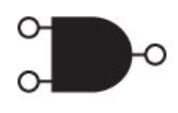
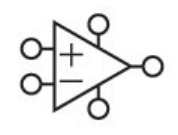

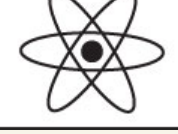
# Introduction to Digital Design

- The Digital Abstraction
- Number Systems
- Logic Gates
- Beneath the Digital Abstraction




Chap 1

# The Digital Abstraction

Application Software		Programs
Operating Systems		Device Drivers
Architecture		Instructions Registers
Micro-architecture		Datapaths Controllers
Logic		Adders Memories
Digital Circuits		AND Gates NOT Gates
Analog Circuits		Amplifiers Filters
Devices		Transistors Diodes
Physics		Electrons

 - The Three -Y's
  - Hierarchy
    - » A system divided into modules and submodules
  - Modularity
    - » Having well-defined functions and interfaces
  - Regularity
    - » Encouraging uniformity, so modules can be easily reused
- Positive voltage is commonly used to represent '1' and zero volt to represent '0'



# Number Systems

- Decimal Numbers
- Binary Numbers
- Hexadecimals Numbers

1's column  
10's column  
100's column  
1000's column

$$9742_{10} = 9 \times 10^3 + 7 \times 10^2 + 4 \times 10^1 + 2 \times 10^0$$

nine thousands      seven hundreds      four tens      two ones

1's column  
2's column  
4's column  
8's column  
16's column

$$10110_2 = 1 \times 2^4 + 0 \times 2^3 + 1 \times 2^2 + 1 \times 2^1 + 0 \times 2^0 = 22_{10}$$

one sixteen      no eight      one four      one two      no one

1's column  
16's column  
256's column

$$2ED_{16} = 2 \times 16^2 + E \times 16^1 + D \times 16^0 = 749_{10}$$

two two hundred fifty six's      fourteen sixteens      thirteen ones

- Decimal to Binary Conversion

**Method 1:** Find the largest power of 2 that fits, subtract and repeat

$53_{10}$	$32 \times 1$
$53 - 32 = 21$	$16 \times 1$
$21 - 16 = 5$	$4 \times 1$
$5 - 4 = 1$	$1 \times 1$

$$= 110101_2$$

**Method 2:** Repeatedly divide by 2, remainder goes in next most significant bit

$53_{10} =$	$53/2 = 26$	R1
	$26/2 = 13$	R0
	$13/2 = 6$	R1
	$6/2 = 3$	R0
	$3/2 = 1$	R1
	$1/2 = 0$	R1

$$= 110101_2$$


- Binary Values and Range
  - **$N$ -digit decimal number**
    - How many values?  $10^N$
    - Range?  $[0, 10^N - 1]$
    - Example: 3-digit decimal number:
      - $10^3 = 1000$  possible values
      - Range:  $[0, 999]$
  - **$N$ -bit binary number**
    - How many values?  $2^N$
    - Range:  $[0, 2^N - 1]$
    - Example: 3-digit binary number:
      - $2^3 = 8$  possible values
      - Range:  $[0, 7] = [000_2 \text{ to } 111_2]$

Hex Digit	Decimal	Binary
0	0	0000
1	1	0001
2	2	0010
3	3	0011
4	4	0100
5	5	0101
6	6	0110
7	7	0111
8	8	1000
9	9	1001
A	10	1010
B	11	1011
C	12	1100
D	13	1101
E	14	1110
F	15	1111

- Hexadecimal to Binary Conversion
  - Hexadecimal to binary conversion:
    - Convert  $4AF_{16}$  (also written  $0x4AF$ ) to binary
    - $0100\ 1010\ 1111_2$
  - Hexadecimal to decimal conversion:
    - Convert  $4AF_{16}$  to decimal
    - $16^2 \times 4 + 16^1 \times 10 + 16^0 \times 15 = 1199_{10}$



- Byte, Word, MSB, LSB

 

- Estimating Powers of Two

- $2^{10} = 1 \text{ kilo} \approx 1000 \text{ (1024)}$
- $2^{20} = 1 \text{ mega} \approx 1 \text{ million (1,048,576)}$
- $2^{30} = 1 \text{ giga} \approx 1 \text{ billion (1,073,741,824)}$

- What is the value of  $2^{24}$ ?

$$2^4 \times 2^{20} \approx 16 \text{ million}$$

- How many values can a 32-bit variable represent?

$$2^2 \times 2^{30} \approx 4 \text{ billion}$$



- Binary Addition

<div style="display: flex; justify-content: space-around; align-items: center;"> <div style="text-align: center;"> <math display="block">  \begin{array}{r}  11 \\  4277 \\  + 5499 \\  \hline  9776  \end{array}  </math> </div> <div style="text-align: center;"> <math>\leftarrow \text{carries} \rightarrow</math> </div> <div style="text-align: center;"> <math display="block">  \begin{array}{r}  11 \\  1011 \\  + 0011 \\  \hline  1110  \end{array}  </math> </div> </div> <div style="display: flex; justify-content: space-around; margin-top: 10px;"> <span><b>(a)</b></span> <span><b>(b)</b></span> </div>
--

$  \begin{array}{r}  11 \quad 1 \\  1101 \\  + 0101 \\  \hline  10010  \end{array}  $
---

- Overflow

» when result is too big to fit in the available number of bits

$$\begin{array}{r}
 111 \\
 1011 \\
 + 0110 \\
 \hline
 10001
 \end{array}$$

- Signed Binary Numbers

- Sign and Magnitude

- 1 sign bit,  $N-1$  magnitude bits
    - Sign bit is the most significant (left-most) bit
      - Positive number: sign bit = 0
      - Negative number: sign bit = 1

$$A: \{a_{N-1}, a_{N-2}, \dots, a_2, a_1, a_0\}$$

$$A = (-1)^{a_{N-1}} \sum_{i=0}^{N-2} a_i 2^i$$

- Example, 4-bit sign/mag representations of  $\pm 6$ :

+6 = 0110

- 6 = 1110

- Range of an  $N$ -bit sign/magnitude number:

$[-(2^{N-1}-1), 2^{N-1}-1]$

### Problems:

- Addition doesn't work, for example  $-6 + 6$ :

1110

+ 0110

10100 (wrong!)

- Two representations of 0 ( $\pm 0$ ):

1000

0000

## - Two's Complement

- msb has value of  $-2^{N-1}$

$$A = a_{N-1}(-2^{N-1}) + \sum_{i=0}^{N-2} a_i 2^i$$

- Most positive 4-bit number: **0111**
- Most negative 4-bit number: **1000**
- The most significant bit still indicates the sign (1 = negative, 0 = positive)
- Range of an  $N$ -bit two's complement number:

$$[-(2^{N-1}), 2^{N-1}-1]$$

### » Taking the Two's Complement

### » Two's Complement Addition

- Add  $6 + (-6)$  using two's complement numbers

$$\begin{array}{r} \textcolor{blue}{111} \\ 0110 \\ + 1010 \\ \hline 10000 \end{array}$$

- Add  $-2 + 3$  using two's complement numbers

$$\begin{array}{r} \textcolor{blue}{111} \\ 1110 \\ + 0011 \\ \hline 10001 \end{array}$$

- “Taking the Two's complement” **flips the sign** of a two's complement number

- **Method:**

1. Invert the bits
2. Add 1

- **Example:** Flip the sign of  $3_{10} = 0011_2$


1. **1100**
2. **+ 1**  
**1101 = -3<sub>10</sub>**

- Sign-Extension

- Sign bit copied to msb's
- Number value is same
- **Example 1:**
  - 4-bit representation of 3 = 0011
  - 8-bit sign-extended value: 00000011
- **Example 2:**
  - 4-bit representation of -5 = 1011
  - 8-bit sign-extended value: 11111011


- Number System Comparison

Number System	Range
Unsigned	$[0, 2^N-1]$
Sign/Magnitude	$[-(2^{N-1}-1), 2^{N-1}-1]$
Two's Complement	$[-2^{N-1}, 2^{N-1}-1]$

 

# Logic Gates


## NOT

 

$$Y = \overline{A}$$

A	Y
0	1
1	0


## BUF

 

$$Y = A$$

A	Y
0	0
1	1


## AND

 

$$Y = AB$$

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1


## OR

 

$$Y = A + B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1


## XOR

 

$$Y = A \oplus B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0


## NAND

 

$$Y = \overline{AB}$$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0


## NOR

 

$$Y = \overline{A + B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

## XNOR

 


$$Y = \overline{A \oplus B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

- Multiple-Input Logic Gates


### NOR3

 

$$Y = \overline{A+B+C}$$

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

### AND3

 


$$Y = ABC$$

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

 
# Beneath the Digital Abstraction

- Logic levels
  - Discrete voltages represent 1 and 0
  - For example:
    - 0 = *ground* (GND) or 0 volts
    - 1 =  $V_{DD}$  or 5 volts
  - What about 4.99 volts? Is that a 0 or a 1?
  - What about 3.2 volts?
- What is Noise ?
  - **Anything that degrades the signal**
    - E.g., resistance, power supply noise, coupling to neighboring wires, etc.
  - **Example:** a gate (driver) outputs 5 V but, because of resistance in a long wire, receiver gets 4.5 V





- Noise Margins

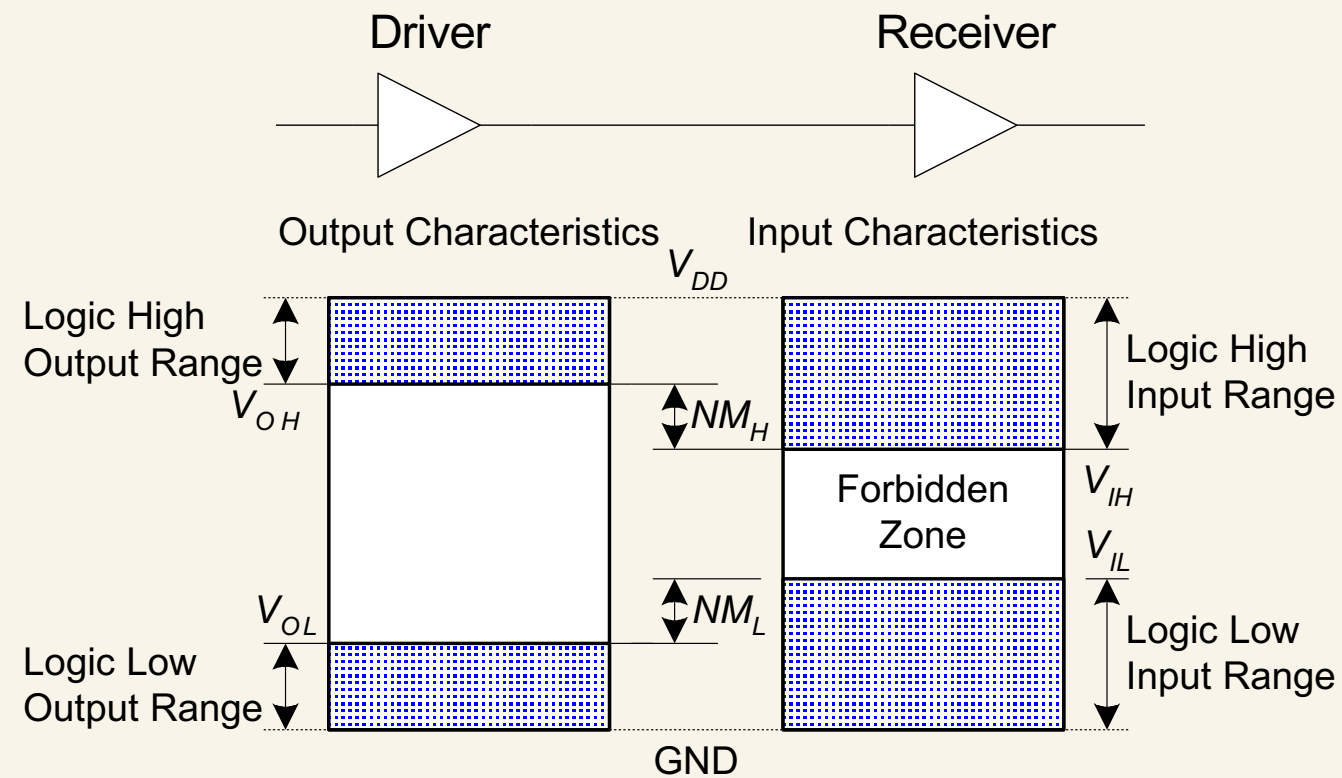


**High Noise Margin:**  $NM_H = V_{OH} - V_{IH}$

**Low Noise Margin:**  $NM_L = V_{IL} - V_{OL}$


- DC Transfer Characteristics

Ideal Buffer:

 


$$NM_H = NM_L = V_{DD}/2$$

Real Buffer:

 

$$NM_H, NM_L < V_{DD}/2$$

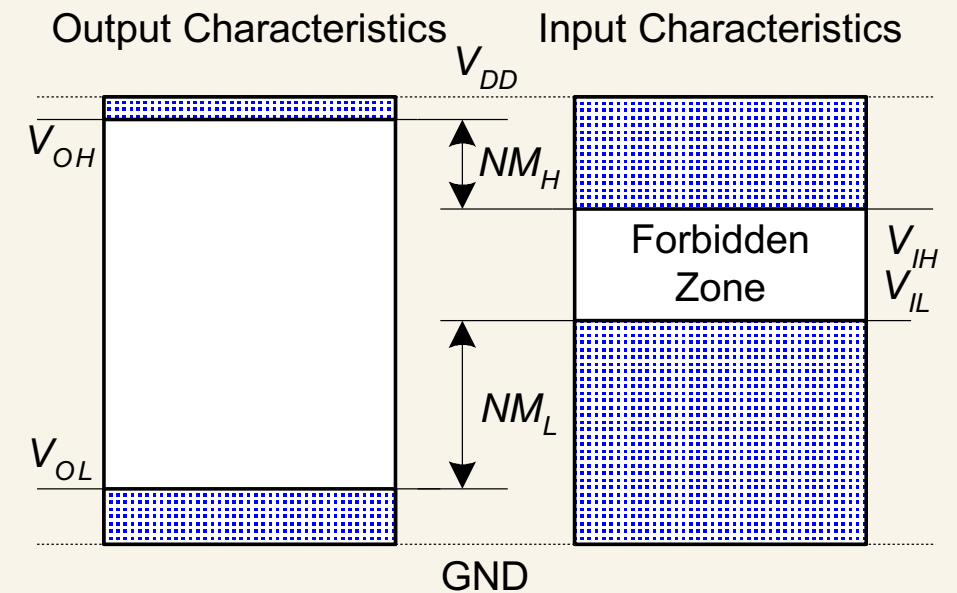


- $V_{DD}$  Scaling

- In 1970's and 1980's,  $V_{DD} = 5\text{ V}$
- $V_{DD}$  has dropped
  - Avoid frying tiny transistors
  - Save power
- 3.3 V, 2.5 V, 1.8 V, 1.5 V, 1.2 V, 1.0 V, ...
  - Be careful connecting chips with different supply voltages



Logic Family	$V_{DD}$	$V_{IL}$	$V_{IH}$	$V_{OL}$	$V_{OH}$
<b>TTL</b>	5 (4.75 - 5.25)	0.8	2.0	0.4	2.4
<b>CMOS</b>	5 (4.5 - 6)	1.35	3.15	0.33	3.84
<b>LVTTL</b>	3.3 (3 - 3.6)	0.8	2.0	0.4	2.4
<b>LVC MOS</b>	3.3 (3 - 3.6)	0.9	1.8	0.36	2.7
 
# • Transistors

- Logic gates built from transistors
- 3-ported voltage-controlled switch
  - 2 ports connected depending on voltage of 3rd
  - d and s are connected (ON) when g is 1



  
- Transistors built from silicon, a semiconductor
- Pure silicon is a poor conductor (no free charges)
- Doped silicon is a good conductor (free charges)
  - n-type (free **negative** charges, electrons)
  - p-type (free **positive** charges, holes)



- nMOS Transistors

 
### Gate = 0

**OFF** (no connection between source and drain)


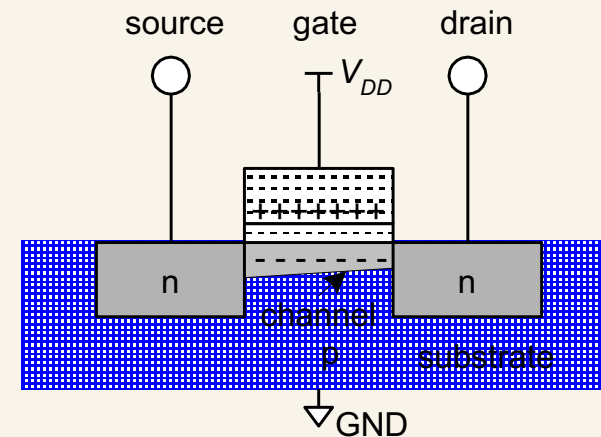
### Gate = 1



**ON** (channel between source and drain)



- pMOS Transistors

  
**pMOS transistor is opposite**

- **ON** when **Gate = 0**
- **OFF** when **Gate = 1**



 
# Gate Implementation

- **nMOS**: pass good **0**'s, so connect source to GND
- **pMOS**: pass good **1**'s, so connect source to  $V_{DD}$




$$Y = \overline{A}$$



A	Y
0	1
1	0

 

A	P1	N1	Y
0	ON	OFF	1
1	OFF	ON	0



 





 
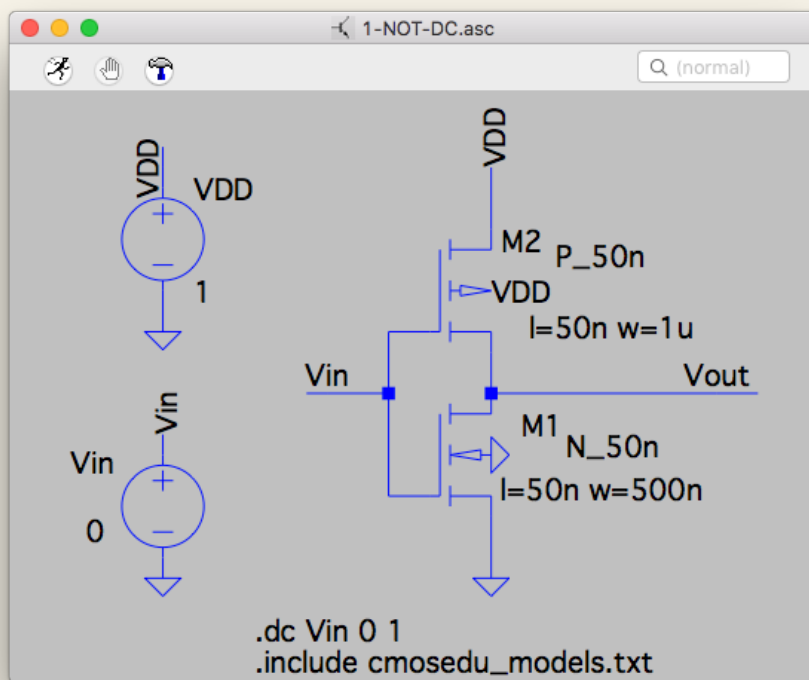
- Gate Simulation
  - 50 nm CMOS
  - $V_{DD} = 1\text{ V}$
  - 2 parameters : L (long) W (Width)
    - »  $L_n = 50\text{ nm}$ ,  $W_n = 500\text{ nm}$
    - »  $L_p = 50\text{ nm}$ ,  $W_p = 2 W_n$
  - Transfer Characteristics :






## - Switching Characteristics

  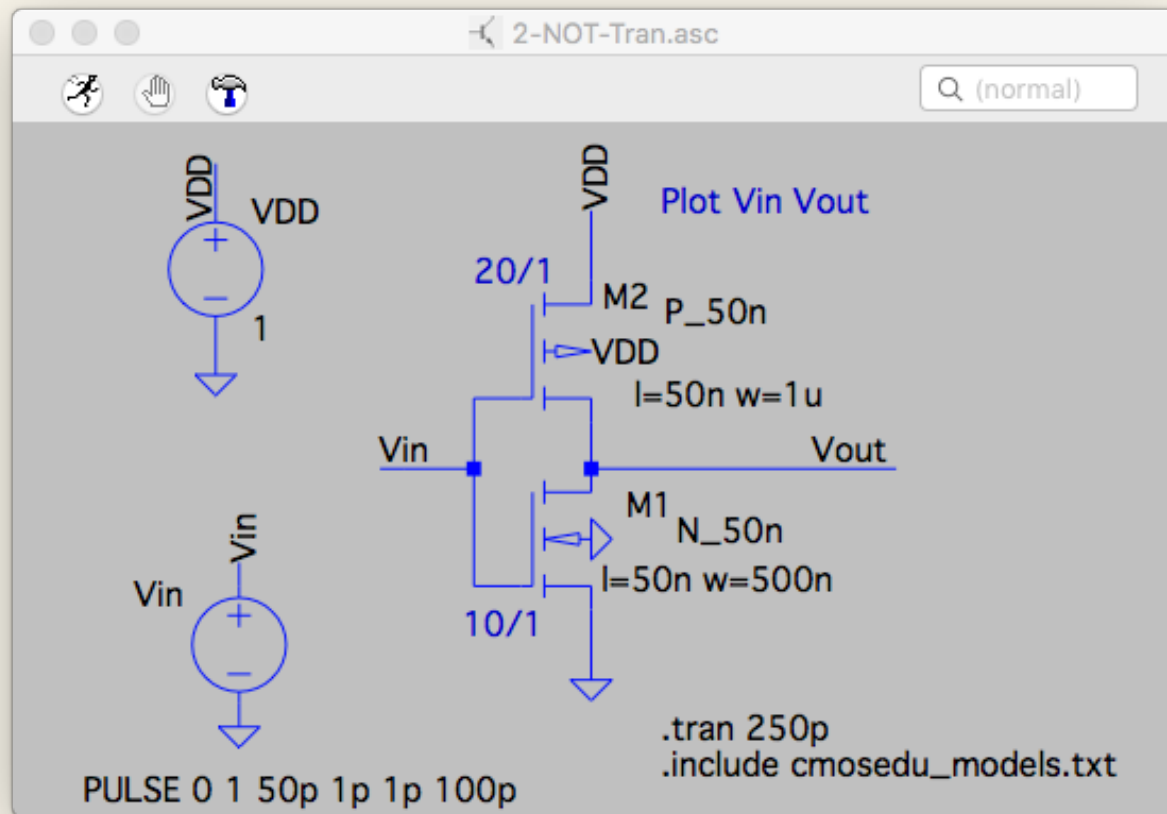

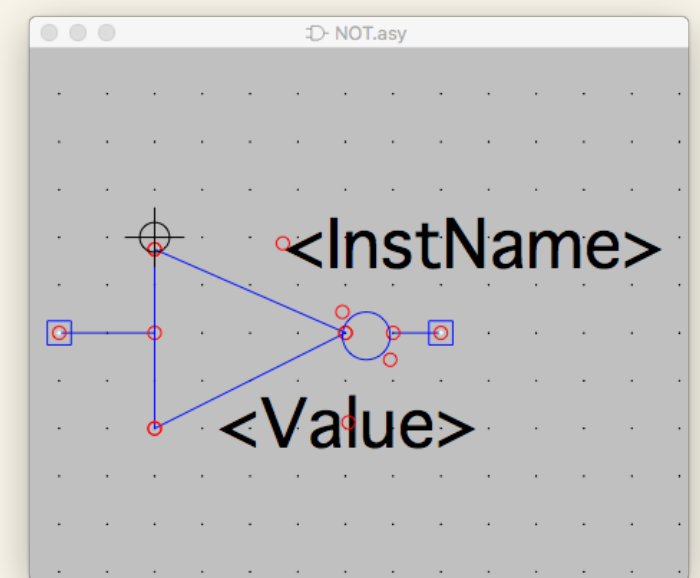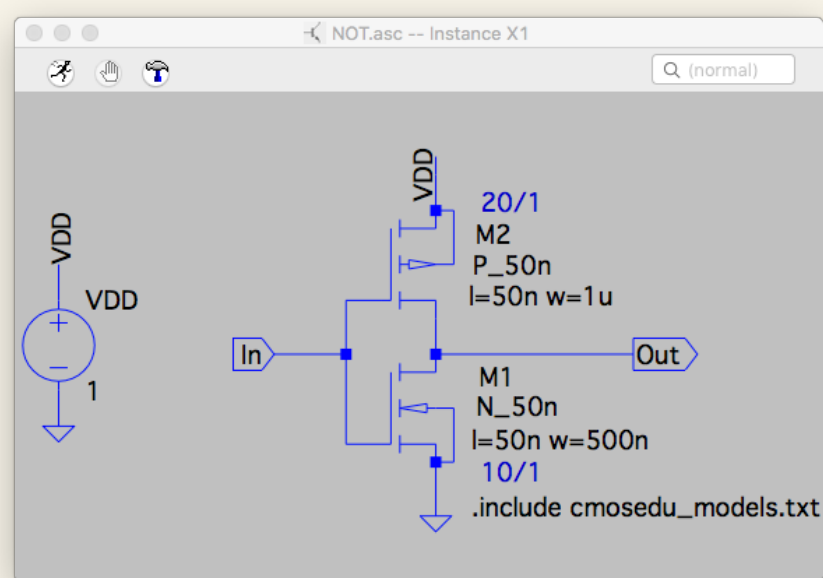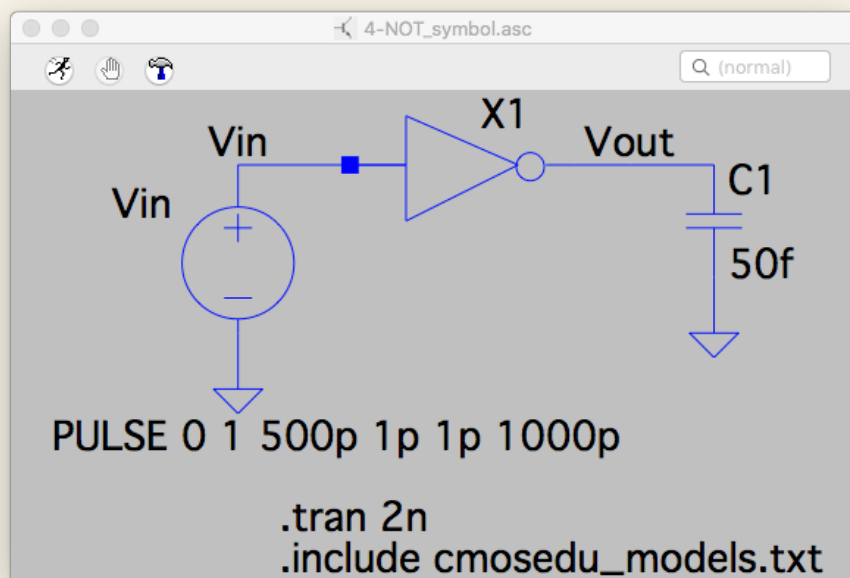 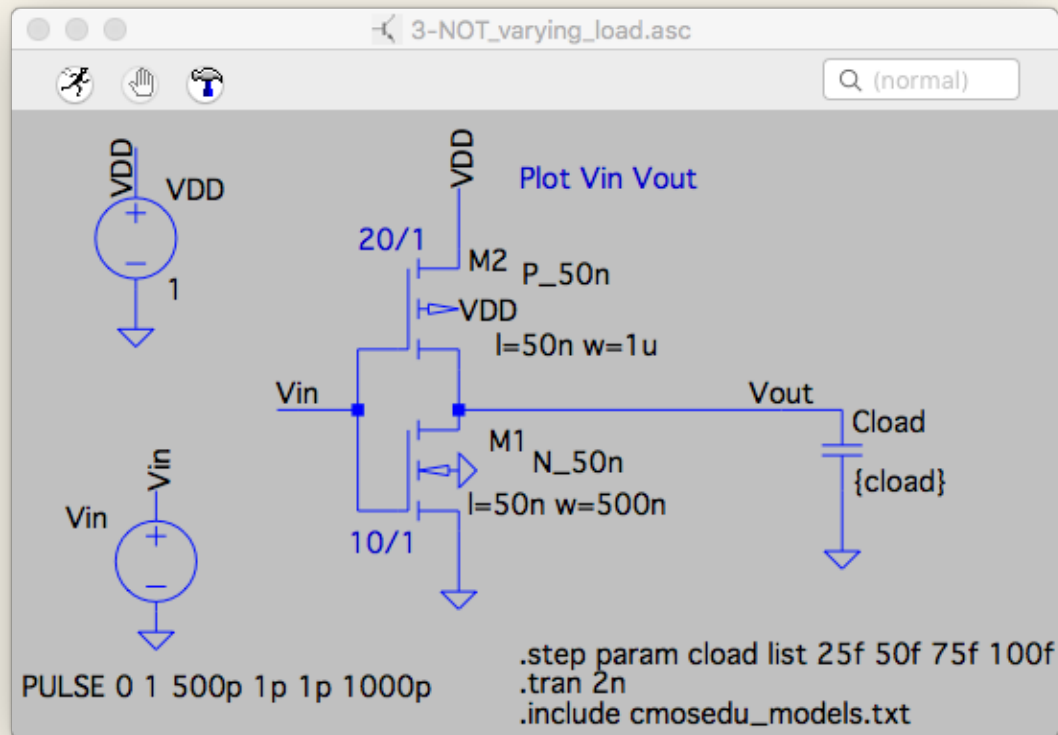


## - NAND

### NAND


 




$$Y = \overline{AB}$$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0



 


A	B	P1	P2	N1	N2	Y
0	0	ON	ON	OFF	OFF	1
0	1	ON	OFF	OFF	ON	1
1	0	OFF	ON	ON	OFF	1
1	1	OFF	OFF	ON	ON	0



 
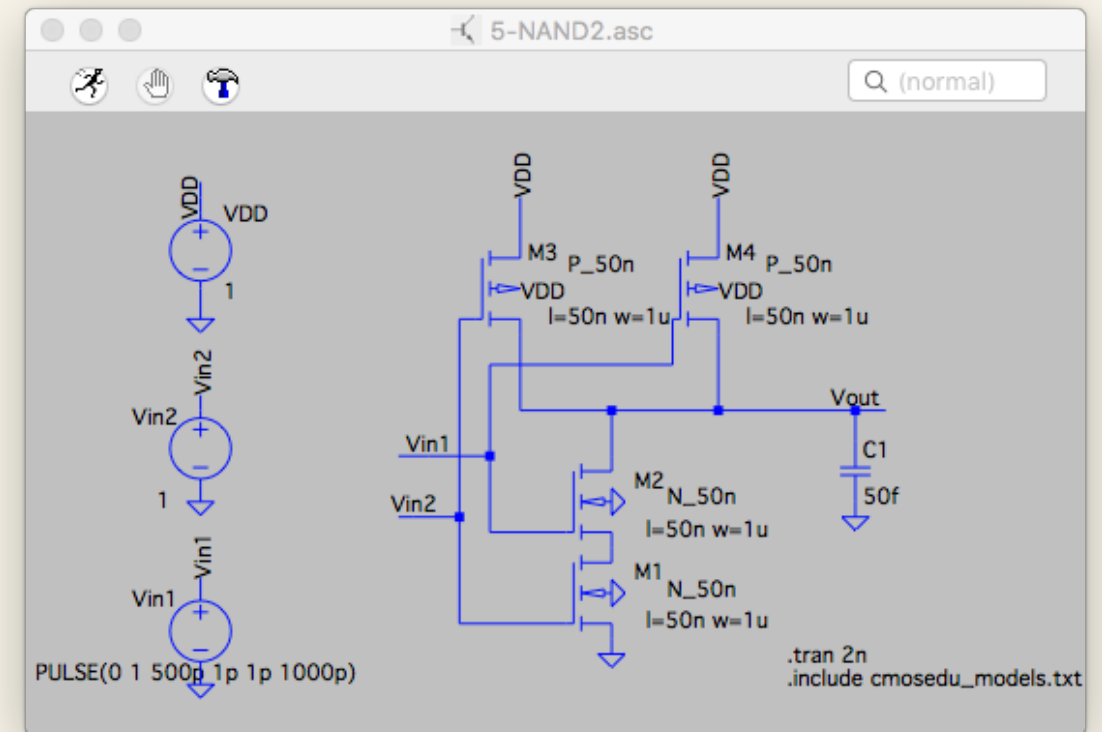


 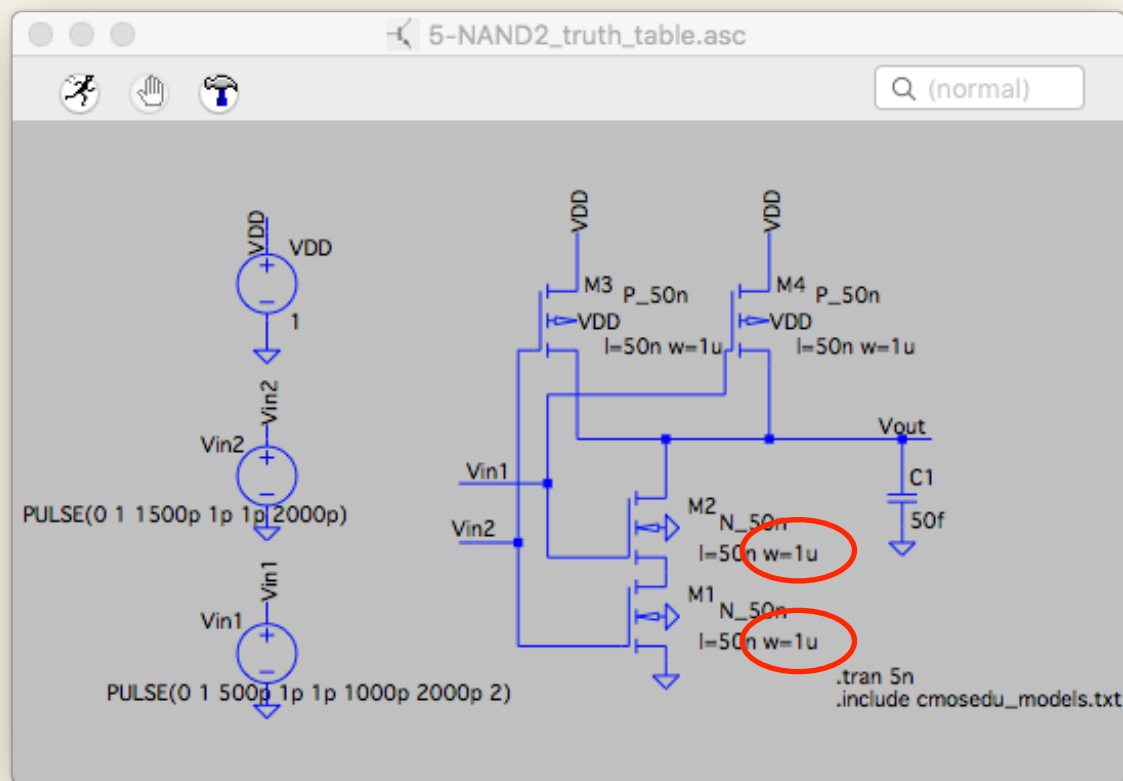

- AND

 
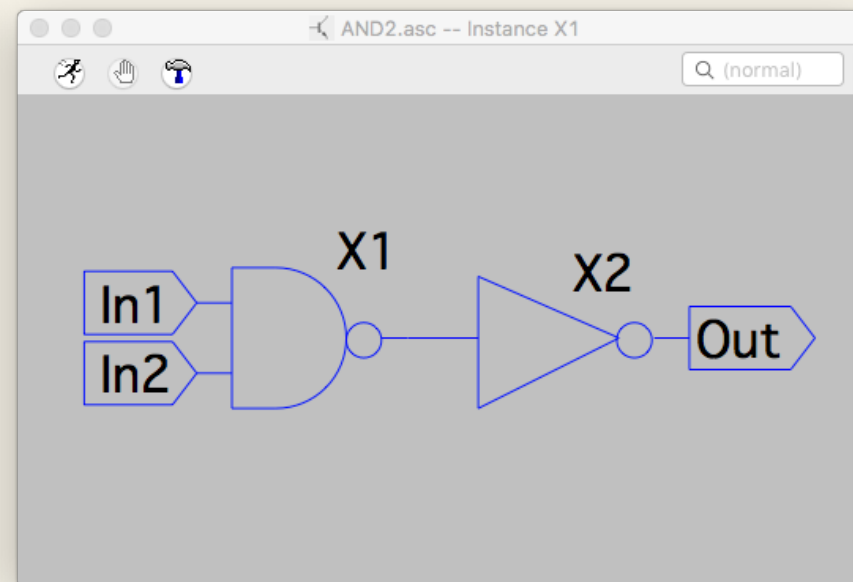
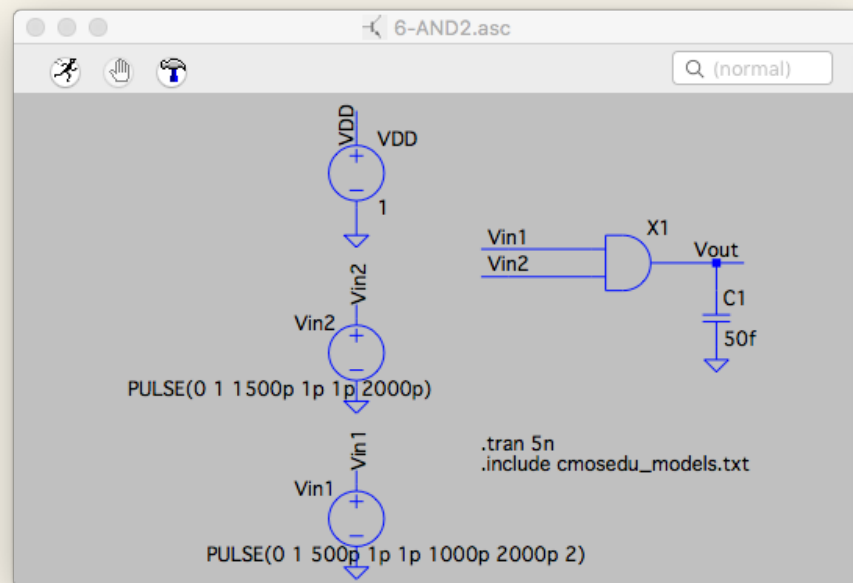






# - NOR

  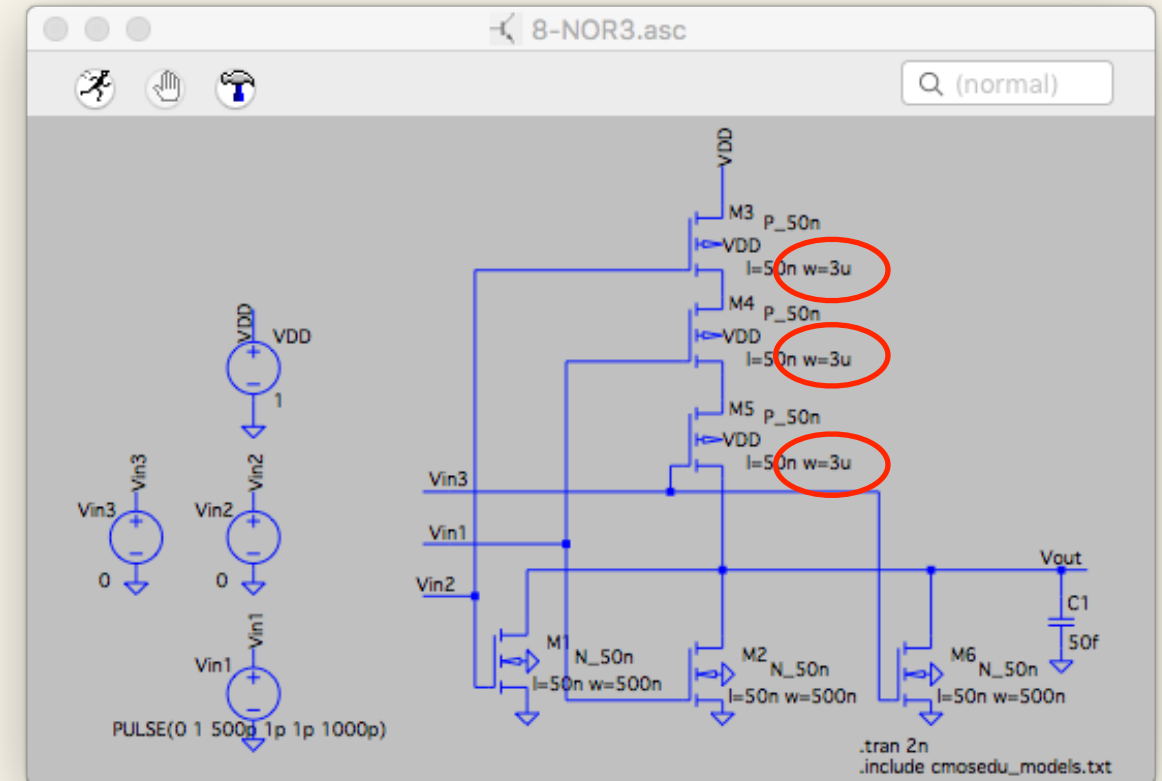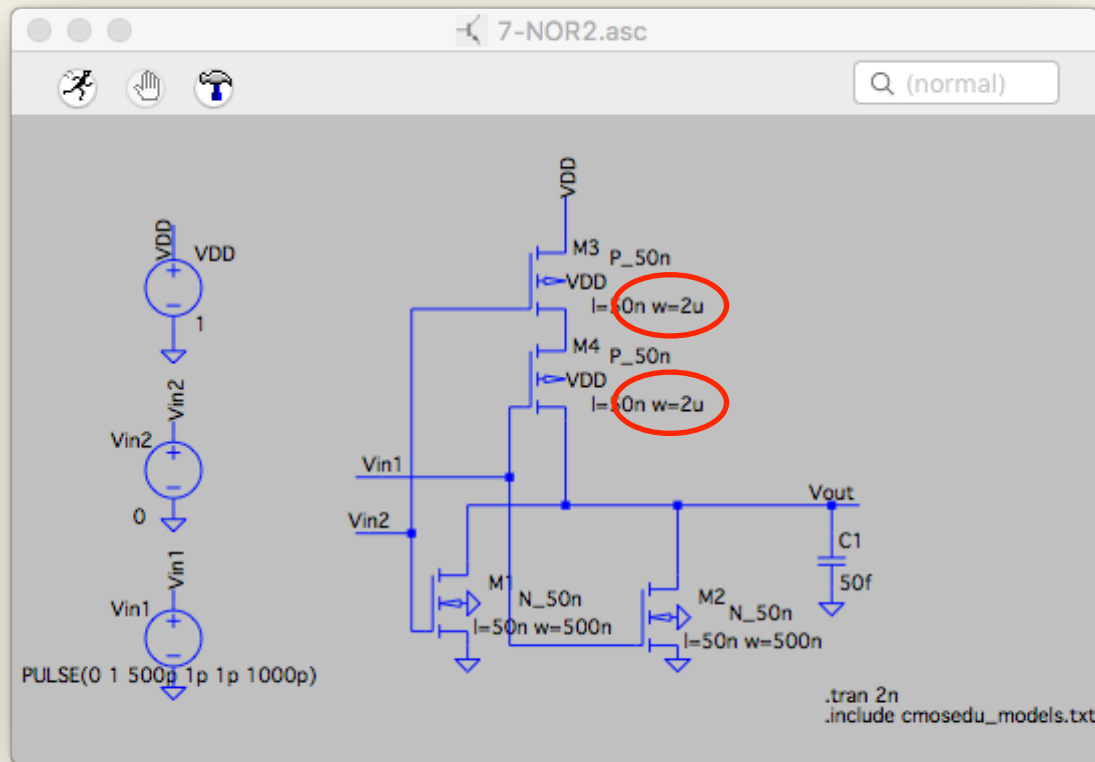
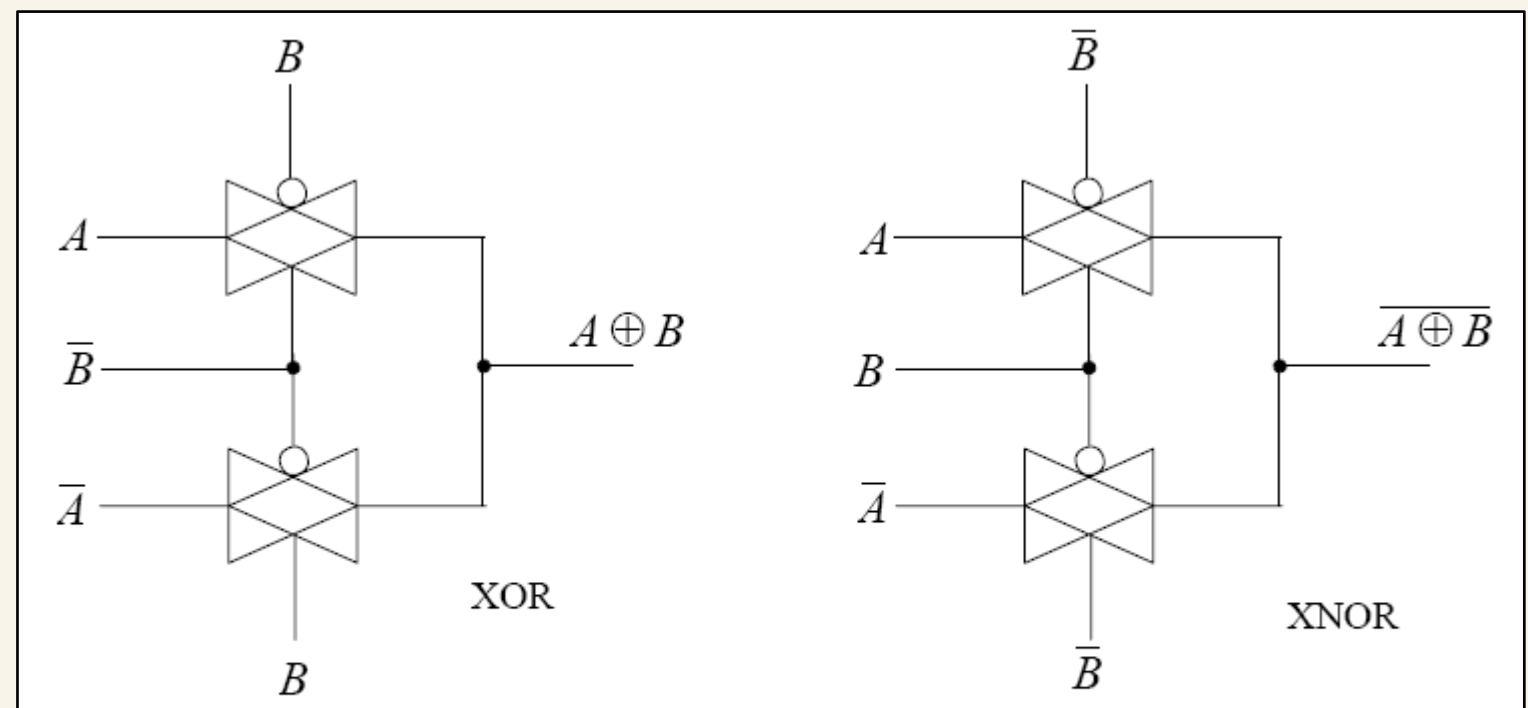  
## • Transmission Gates

- nMOS pass 1's poorly
- pMOS pass 0's poorly
- Transmission gate is a better switch
  - passes both 0 and 1 well
- When  $EN = 1$ , the switch is ON:
  - $EN = 0$  and  $A$  is connected to  $B$
- When  $EN = 0$ , the switch is OFF:
  - $A$  is not connected to  $B$





  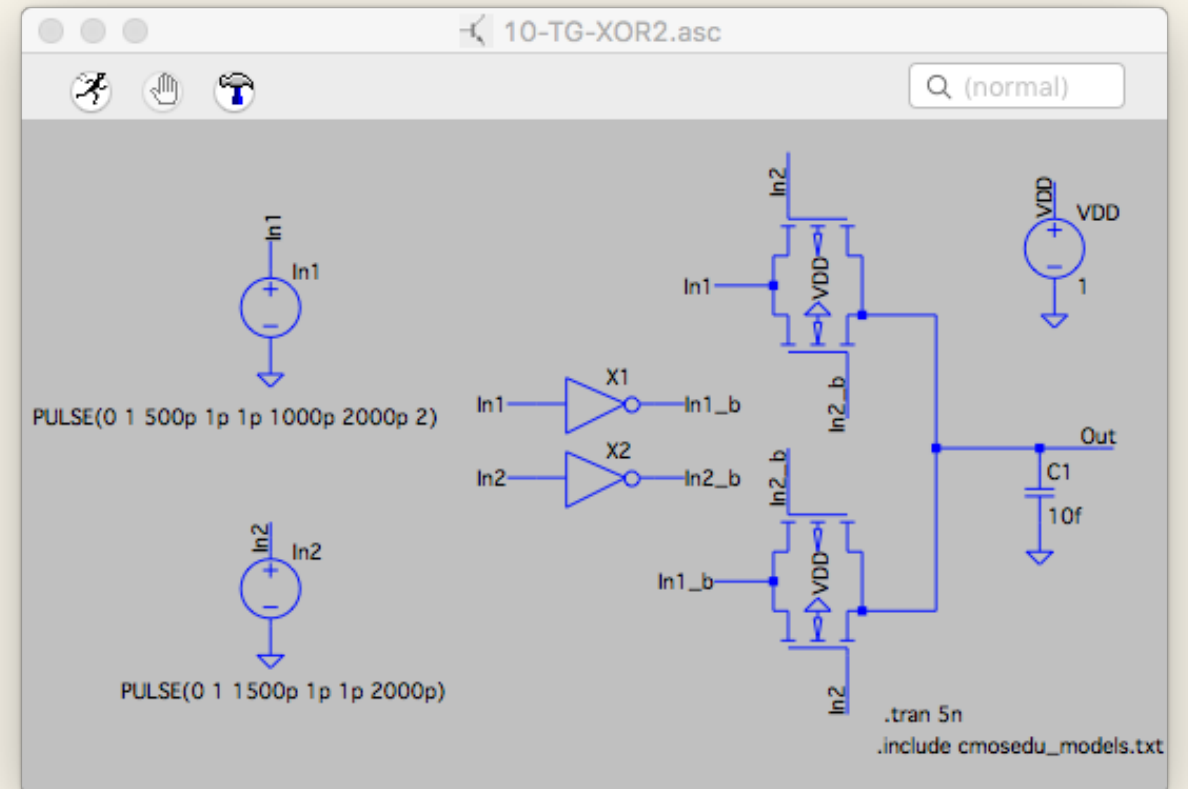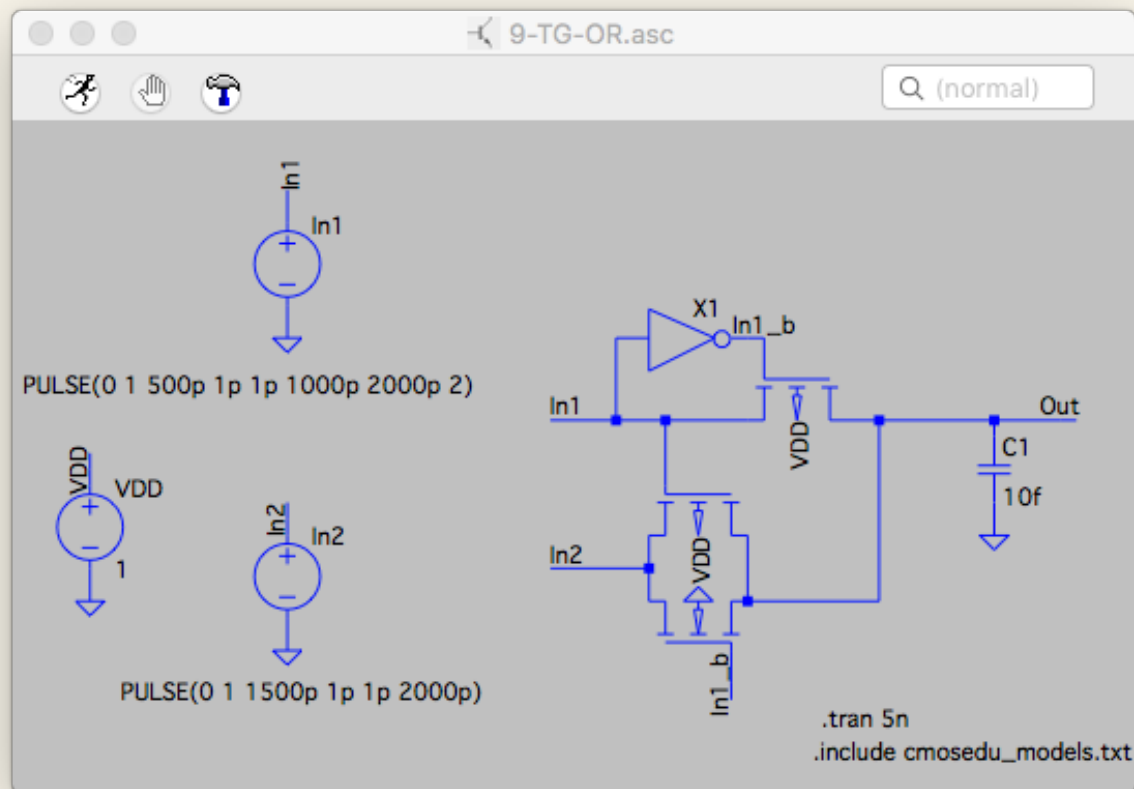



- Pseudo-nMOS Gates

  - Replace pull-up network with *weak* pMOS transistor that is always on
- pMOS transistor: pulls output HIGH *only* when nMOS network not pulling it LOW



- Power Consumption

**Power = Energy consumed per unit time**

- Dynamic power consumption
- Static power consumption

- **Power to charge transistor gate capacitances**

- Energy required to charge a capacitance,  $C$ , to  $V_{DD}$  is  $CV_{DD}^2$
- Circuit running at frequency  $f$ : transistors switch (from 1 to 0 or vice versa) at that frequency
- Capacitor is charged  $f/2$  times per second (discharging from 1 to 0 is free)

- **Dynamic power consumption:**

$$P_{dynamic} = \frac{1}{2}CV_{DD}^2f$$

- Power consumed when no gates are switching
- Caused by the *quiescent supply current*,  $I_{DD}$  (also called the *leakage current*)
- Static power consumption:

$$P_{static} = I_{DD}V_{DD}$$

- Estimate the power consumption of a wireless handheld computer

- $V_{DD} = 1.2 \text{ V}$
- $C = 20 \text{ nF}$
- $f = 1 \text{ GHz}$
- $I_{DD} = 20 \text{ mA}$

$$\begin{aligned} P &= \frac{1}{2}CV_{DD}^2f + I_{DD}V_{DD} \\ &= \frac{1}{2}(20 \text{ nF})(1.2 \text{ V})^2(1 \text{ GHz}) + (20 \text{ mA})(1.2 \text{ V}) \\ &= (14.4 + 0.024) \text{ W} \approx 14.4 \text{ W} \end{aligned}$$